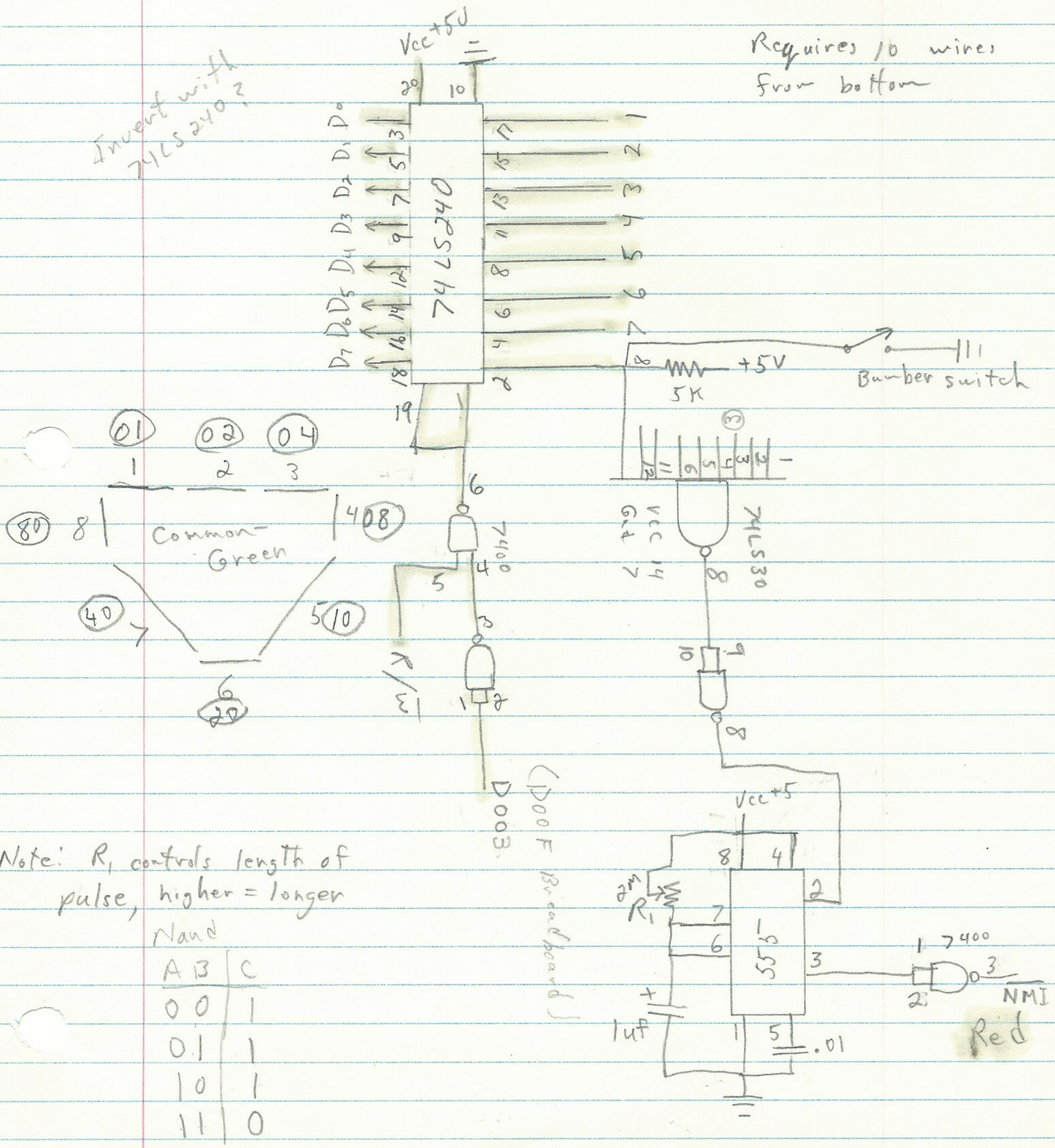


Bamber Interface

Note: all 8 bamber switch are wired the same as example

Invert with 74LS240?

Requires 10 wires from bottom



Note: R₁ controls length of pulse, higher = longer

Nand